



# Learn Git and GitHub without any code!


Using the Hello World guide, you'll start a branch, write comments, and open a pull request.

Read the guide

 [xbarto0c](#) / [Digital-electronics-1](#)

<> Code

! Issues

 Pull requests

 Actions

 Projects

 Wiki

...

 main ▾

[Digital-electronics-1](#) / [Labs](#) / [02-logic](#) /

...



xbarto0c 2.cv ...

2 minutes ago  History

..



images

5 minutes ago



readme.md

2 minutes ago

readme.md



## Binary comparator truth table:

Dec. equivalent	B[1:0]	A[1:0]	B is greater than A	B equals A	B is less than A
0	0 0	0 0	0	1	0
1	0 0	0 1	0	0	1
2	0 0	1 0	0	0	1
3	0 0	1 1	0	0	1

Dec. equivalent	B[1:0]	A[1:0]	B is greater than A	B equals A	B is less than A
4	0 1	0 0	1	0	0
5	0 1	0 1	0	1	0
6	0 1	1 0	0	0	1
7	0 1	1 1	0	0	1
8	1 0	0 0	1	0	0
9	1 0	0 1	1	0	0
10	1 0	1 0	0	1	0
11	1 0	1 1	0	0	1
12	1 1	0 0	1	0	0
13	1 1	0 1	1	0	0
14	1 1	1 0	1	0	0
15	1 1	1 1	0	1	0

## 2-bit Comparator

$f_{b>a\_SoP\_min}$

$a_1 a_0$

	00	01	11	10
00	0	0	0	0
01	1	1	0	0
11	1	1	1	0
10	1	1	1	0

$b_1 b_0$

$f_{b>a\_SoP\_min} = (b_1 \cdot \bar{a}_1) + (\bar{a}_0 b_1 b_0) + (b_0 \bar{a}_1 \bar{a}_0)$

$f_{b<a\_PoS\_min}$

$a_1 a_0$

	00	01	11	10
00	0	1	1	1
01	0	0	1	1
11	0	0	0	0
10	0	0	1	0

$b_1 b_0$

$f_{b<a\_PoS\_min} = (\bar{b}_1 + a_1) \cdot (\bar{b}_0 + a_1) \cdot (a_1 + a_0) \cdot (\bar{b}_1 + \bar{b}_0) \cdot (a_0 + \bar{b}_1)$

$f_{b=a}$

$a_1 a_0$

	00	01	11	10
00	1	0	0	0
01	0	1	0	0
11	0	0	1	0
10	0	0	0	1

$b_1 b_0$

## 4-bit Comparator

## design.vhd

```

-----

library ieee;
use ieee.std_logic_1164.all;

-----

-- Entity declaration for 4-bit binary comparator
-----

entity comparator_4bit is
    port(
        a_i          : in  std_logic_vector(4 - 1 downto 0);
        b_i          : in  std_logic_vector(4 - 1 downto 0);
        -- vektor dvou vodicu

        B_less_A_o    : out std_logic;          -- B is less than A
        B_equals_A_o   : out std_logic;         -- B equals A
        B_greater_A_o : out std_logic          -- B is greater than A
    );
end entity comparator_4bit;

-----

-- Architecture body for 4-bit binary comparator
-----

architecture Behavioral of comparator_4bit is
begin

    B_less_A_o    <= '1' when (b_i < a_i) else '0';
    B_equals_A_o   <= '1' when (b_i = a_i) else '0';
    B_greater_A_o  <= '1' when (b_i > a_i) else '0';

end architecture Behavioral;

```

## testbench.vhd

```

-----

library ieee;
use ieee.std_logic_1164.all;

-----

-- Entity declaration for testbench
-----

entity tb_comparator_4bit is
    -- Entity of testbench is always empty
end entity tb_comparator_4bit;

-----

```

```

-- Architecture body for testbench
-----
architecture testbench of tb_comparator_4bit is

    -- Local signals
    signal s_a      : std_logic_vector(4 - 1 downto 0);
    signal s_b      : std_logic_vector(4 - 1 downto 0);
    signal s_B_greater_A : std_logic;
    signal s_B_equals_A  : std_logic;
    signal s_B_less_A    : std_logic;

begin
    -- Connecting testbench signals with comparator_4bit entity (Unit Under Test)
    uut_comparator_4bit : entity work.comparator_4bit
        port map(
            a_i      => s_a,
            b_i      => s_b,
            B_greater_A_o => s_B_greater_A,
            B_equals_A_o  => s_B_equals_A,
            B_less_A_o    => s_B_less_A
        );

    -----
    -- Data generation process
    -----
    p_stimulus : process
    begin
        -- Report a note at the beginning of stimulus process
        report "Stimulus process started" severity note;

        -- First test values
        s_b <= "0000"; s_a <= "0000"; wait for 100 ns;
        -- Expected output
        assert ((s_B_greater_A = '0') and (s_B_equals_A = '1') and (s_B_less_A = '0'))
        -- If false, then report an error
        report "Test failed for input combination: 0000, 0000" severity error;

        s_b <= "0000"; s_a <= "0001"; wait for 100 ns;
        -- Expected output
        assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A = '0'))
        -- If false, then report an error
        report "Test failed for input combination: 0000, 0001" severity error;

        s_b <= "0000"; s_a <= "0010"; wait for 100 ns;
        -- Expected output
        assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A = '0'))
        -- If false, then report an error
        report "Test failed for input combination: 0000, 0010" severity error;

        s_b <= "0000"; s_a <= "0011"; wait for 100 ns;
        -- Expected output

```

```

    assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0000, 0011" severity error;

s_b <= "0000"; s_a <= "0100"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0000, 0100" severity error;

s_b <= "0000"; s_a <= "0101"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0000, 0101" severity error;

s_b <= "0000"; s_a <= "0110"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0000, 0110" severity error;

s_b <= "0000"; s_a <= "0111"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0000, 0111" severity error;

s_b <= "0000"; s_a <= "1000"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '0') and (s_B_equals_A = '1') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0000, 1000" severity error;

s_b <= "0000"; s_a <= "1001"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0000, 1001" severity error;

-- WRITE OTHER TESTS HERE

-- Report a note at the end of stimulus process
report "Stimulus process finished" severity note;
wait;
end process p_stimulus;

end architecture testbench;

```

## Console error:

```
[2021-02-17 08:53:38 EST] ghdl -i design.vhd testbench.vhd && ghdl -m
tb_comparator_4bit && ghdl -r tb_comparator_4bit --vcd=dump.vcd && sed
-i 's/^U/X/g; s/^-/X/g; s/^H/1/g; s/^L/0/g' dump.vcd
analyze design.vhd
analyze testbench.vhd
elaborate tb_comparator_4bit
testbench.vhd:51:9:@0ms:(report note): Stimulus process started
testbench.vhd:105:9:@900ns:(assertion error): Test failed for input
combination: 0000, 1000
testbench.vhd:119:9:@1us:(report note): Stimulus process finished
Finding VCD file...
./dump.vcd
[2021-02-17 08:53:39 EST] Opening EPWave...
Done
```

[EDA playground link](#)