



Learn Git and GitHub without any code!

Using the Hello World guide, you'll start a branch, write comments, and open a pull request.

Read the guide

xbarto0c / Digital-electronics-1

<> Code

! Issues

🔗 Pull requests

▶ Actions

📁 Projects

📖 Wiki

🛡️ Security

🔑 main ▾

Digital-electronics-1 / Labs / 02-logic /



xbarto0c 2.cv ...

yesterday 🕒 History

..



images

yesterday



readme.md

yesterday



readme.pdf

yesterday

readme.md



Binary comparator truth table:

Dec. equivalent	B[1:0]	A[1:0]	B is greater than A	B equals A	B is less than A
0	0 0	0 0	0	1	0
1	0 0	0 1	0	0	1
2	0 0	1 0	0	0	1

Dec. equivalent	B[1:0]	A[1:0]	B is greater than A	B equals A	B is less than A
3	0 0	1 1	0	0	1
4	0 1	0 0	1	0	0
5	0 1	0 1	0	1	0
6	0 1	1 0	0	0	1
7	0 1	1 1	0	0	1
8	1 0	0 0	1	0	0
9	1 0	0 1	1	0	0
10	1 0	1 0	0	1	0
11	1 0	1 1	0	0	1
12	1 1	0 0	1	0	0
13	1 1	0 1	1	0	0
14	1 1	1 0	1	0	0
15	1 1	1 1	0	1	0

2-bit Comparator

$f_{b>a_SoP_min}$

$a_1 a_0$

	00	01	11	10
$b_1 b_0$	00	0	0	0
	01	1	0	0
	11	1	1	0
	10	1	1	0

$f_{b>a_SoP_min} = (b_1 \cdot \bar{a}_1) + (\bar{a}_0 b_1 b_0) + (b_0 \bar{a}_1 \bar{a}_0)$

$f_{b<a_PoS_min}$

$a_1 a_0$

	00	01	11	10
$b_1 b_0$	00	0	1	1
	01	0	0	1
	11	0	0	0
	10	0	0	1

$f_{b<a_PoS_min} = (\bar{b}_1 + a_1) \cdot (\bar{b}_0 + a_1) \cdot (a_1 + a_0) \cdot (\bar{b}_1 + \bar{b}_0) \cdot (a_0 + b_1)$

$f_{b=a}$

$a_1 a_0$

	00	01	11	10
$b_1 b_0$	00	1	0	0
	01	0	1	0
	11	0	0	1
	10	0	0	1

4-bit Comparator

design.vhd

```

-----

library ieee;
use ieee.std_logic_1164.all;

-----

-- Entity declaration for 4-bit binary comparator
-----

entity comparator_4bit is
    port(
        a_i          : in  std_logic_vector(4 - 1 downto 0);
        b_i          : in  std_logic_vector(4 - 1 downto 0);
        -- vektor dvou vodicu

        B_less_A_o    : out std_logic;          -- B is less than A
        B_equals_A_o  : out std_logic;          -- B equals A
        B_greater_A_o : out std_logic           -- B is greater than A
    );
end entity comparator_4bit;

-----

-- Architecture body for 4-bit binary comparator
-----

architecture Behavioral of comparator_4bit is
begin

    B_less_A_o    <= '1' when (b_i < a_i) else '0';
    B_equals_A_o  <= '1' when (b_i = a_i) else '0';
    B_greater_A_o <= '1' when (b_i > a_i) else '0';

end architecture Behavioral;

```

testbench.vhd

```

-----

library ieee;
use ieee.std_logic_1164.all;

-----

-- Entity declaration for testbench
-----

entity tb_comparator_4bit is
    -- Entity of testbench is always empty
end entity tb_comparator_4bit;

-----

```

```

-- Architecture body for testbench
-----

architecture testbench of tb_comparator_4bit is

    -- Local signals
    signal s_a      : std_logic_vector(4 - 1 downto 0);
    signal s_b      : std_logic_vector(4 - 1 downto 0);
    signal s_B_greater_A : std_logic;
    signal s_B_equals_A  : std_logic;
    signal s_B_less_A    : std_logic;

begin
    -- Connecting testbench signals with comparator_4bit entity (Unit Under Te
    uut_comparator_4bit : entity work.comparator_4bit
        port map(
            a_i      => s_a,
            b_i      => s_b,
            B_greater_A_o => s_B_greater_A,
            B_equals_A_o  => s_B_equals_A,
            B_less_A_o    => s_B_less_A
        );

    -----
    -- Data generation process
    -----

    p_stimulus : process
    begin
        -- Report a note at the beginning of stimulus process
        report "Stimulus process started" severity note;

        -- First test values
        s_b <= "0000"; s_a <= "0000"; wait for 100 ns;
        -- Expected output
        assert ((s_B_greater_A = '0') and (s_B_equals_A = '1') and (s_B_less_A
        -- If false, then report an error
        report "Test failed for input combination: 0000, 0000" severity error;

        s_b <= "0000"; s_a <= "0001"; wait for 100 ns;
        -- Expected output
        assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A
        -- If false, then report an error
        report "Test failed for input combination: 0000, 0001" severity error;

        s_b <= "0000"; s_a <= "0010"; wait for 100 ns;
        -- Expected output
        assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A
        -- If false, then report an error
        report "Test failed for input combination: 0000, 0010" severity error;

        s_b <= "0000"; s_a <= "0011"; wait for 100 ns;
        -- Expected output

```

```

    assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0000, 0011" severity error;

s_b <= "0000"; s_a <= "0100"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0000, 0100" severity error;

s_b <= "0000"; s_a <= "0101"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0000, 0101" severity error;

s_b <= "0000"; s_a <= "0110"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0000, 0110" severity error;

s_b <= "0000"; s_a <= "0111"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0000, 0111" severity error;

s_b <= "0000"; s_a <= "1000"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '0') and (s_B_equals_A = '1') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0000, 1000" severity error;

s_b <= "0000"; s_a <= "1001"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0000, 1001" severity error;

-- WRITE OTHER TESTS HERE

-- Report a note at the end of stimulus process
report "Stimulus process finished" severity note;
wait;
end process p_stimulus;

end architecture testbench;

```

Console error:

```
[2021-02-17 08:53:38 EST] ghdl -i design.vhd testbench.vhd && ghdl -m
tb_comparator_4bit && ghdl -r tb_comparator_4bit --vcd=dump.vcd && sed
-i 's/^U/X/g; s/^-/X/g; s/^H/1/g; s/^L/0/g' dump.vcd
analyze design.vhd
analyze testbench.vhd
elaborate tb_comparator_4bit
testbench.vhd:51:9:@0ms:(report note): Stimulus process started
testbench.vhd:105:9:@900ns:(assertion error): Test failed for input
combination: 0000, 1000
testbench.vhd:119:9:@1us:(report note): Stimulus process finished
Finding VCD file...
./dump.vcd
[2021-02-17 08:53:39 EST] Opening EPWave...
Done
```

EDA playground link:

<https://www.edaplayground.com/x/EQTE>